



VHDL Essentials



VHDL Essentials

Index

- ❑ Things you should know before we start
- ❑ VHDL vs. processor
- ❑ Introduction to VHDL
 - ❑ Signal types
 - ❑ Libraries and operators
 - ❑ Entity
 - ❑ Architecture
 - ❑ Process
 - ❑ Decision and loop statements
 - ❑ Summary example



VHDL Essentials

Things you should know before we start

- ❑ Boolean algebra (logic): AND, OR, etc.
- ❑ Basic combinational digital systems such as
 - ❑ Multiplexer
 - ❑ Encoder, decoder
 - ❑ Comparator
 - ❑ Tri-state buffer
 - ❑ ALU (Arithmetic Logic Unit)
- ❑ Basic sequential digital systems such as
 - ❑ D flip-flop
 - ❑ Data and shift registers
 - ❑ Counters



VHDL Essentials

VHDL vs. processor

With a processor

- 1) Processors are programmed to follow a series of instructions executed in a sequential order
- 2) Given fixed computer architecture
- 3) Single threat in a single processor. *Ex. Perform 4 additions with a PIC*
 - a) Only 1 option: execution of ADD instruction 4 times

With VHDL

- 1) Statements infer digital systems, not instructions in a processor
- 2) There's no processor but a custom-made circuit that employs only the necessary components that execute the intended algorithm
- 3) Flexibility to implement solutions in parallel. *Ex. Perform 4 additions in VHDL*
 - a) Op1: 1 adder 4 times
 - b) Op2: 2 adders 2 times
 - c) Op3: 4 adders 1 time



VHDL Essentials

Introduction to VHDL

- ❑ VHDL = VHSIC + HDL: *Very High Speed Integrated Circuit + Hardware Description Language*
- ❑ Description of hardware circuits with a language
Hardware Description Language (HDL)
- ❑ Circuits can be described based on their functional behavior

```
if A > B then  
    output <= A;  
end if;
```


- ❑ The VHDL synthesizer understands the user's code and infers the corresponding digital system
- ❑ VHDL designs are implemented in FPGA (Field Programmable Gate Array) devices



VHDL Essentials

Introduction to VHDL


- ❑ Lab Software
ISE Xilinx 13.4

 

- ❑ Full version available
in the lab
- ❑ Free demo version

ISE WebPACK can be downloaded with limited capabilities
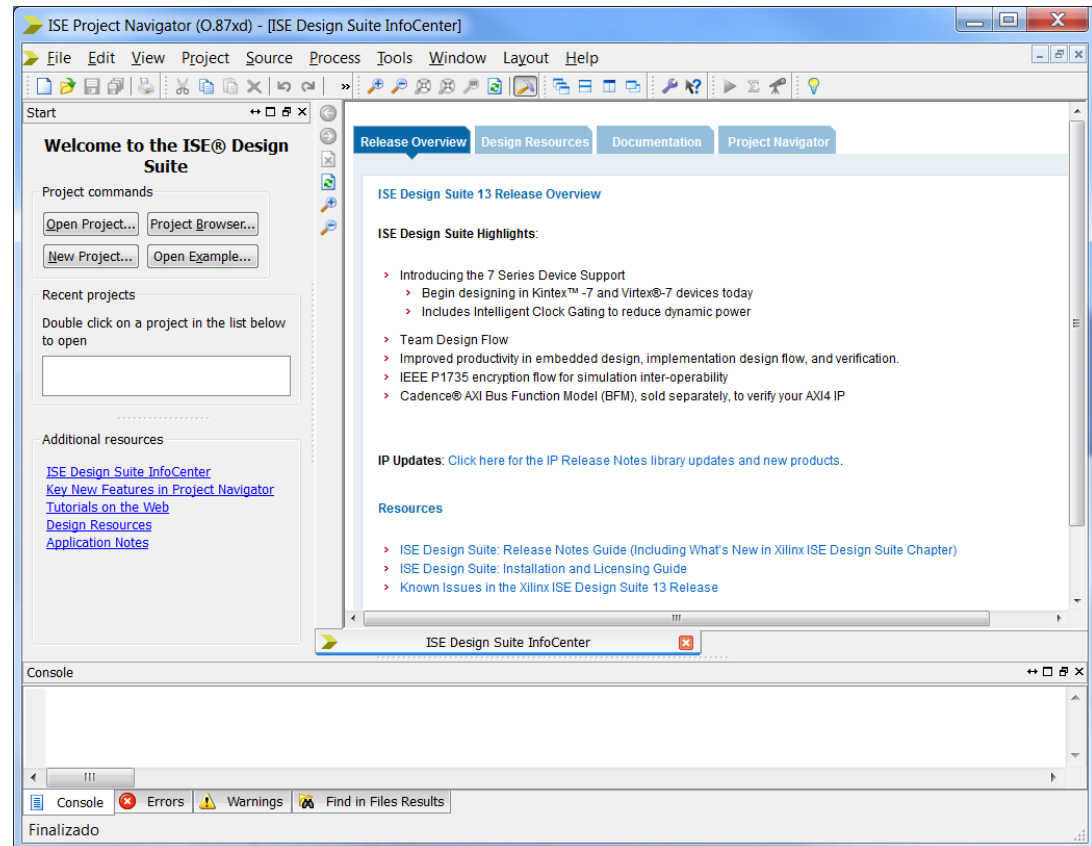
<http://www.xilinx.com/support/download/index.htm>





VHDL Essentials

Signal types

- ❑ VHDL designs have signals that can have logic or arithmetic values
- ❑ Most common signal types:
 - ❑ `Std_logic`: '1'. Bit with '0', '1' or 'Z' (high impedance) value
 - ❑ `Std_logic_vector(3 downto 0)`: "0011". Vector of `std_logic`
 - ❑ `Signed`: -2. Integer with a sign
 - ❑ `Unsigned`: 7. Integer without a sign
- ❑ Normally signals are `std_logic`
- ❑ `Signed` and `unsigned` signals infer buses: 7 = "00000111"
- ❑ Different signal types support different operations
 - ❑ `std_logic` signals do not support arithmetic operations
 - ❑ `signed` or `unsigned` types recommended for arithmetic operations



VHDL Essentials

Libraries and operators

❑ Libraries include definitions of signal types and operations

- ❑ Normally our designs will have only two libraries

```
library ieee;  
use ieee.std_logic_1164.all; -- for logic operations  
use ieee.numeric_std.all;    -- for arithm operations
```

❑ Most common operators

- ❑ Boolean: AND, OR, NOT `out1 <= in1 OR in2;`
- ❑ Arithmetic: +, -, *, /¹ `out1 <= in1 + in2;`
- ❑ Comparison: <, >=, /= `if (in1 /= in2)...`
- ❑ Concatenation (of bits): & `out1<= in1 & in2;`

1 Division is not synthesizable, it can be used only in simulation



VHDL Essentials

Entity

- ❑ **Entity** defines how a design element connects to other VHDL models (its interface) and also defines its name
- ❑ **Ports** are the signals that connect entities, detailing inputs and outputs of our design

```
Entity example is
port (
    in1   : in std_logic; -- input1 port
    in2   : in std_logic; -- input2 port
    out1  : out std_logic); -- output1 port
End example;
```



VHDL Essentials

Architecture

- ❑ **Architecture** describes the behavior of an entity

```
Entity example is
port(
    in1   : in std_logic;
    in2   : in std_logic;
    out1  : out std_logic);
End example;
```

```
Architecture behavior of example is
-- Add here internal signals only visible within this architecture
internal_signal1 : std_logic;

Begin
    internal_signal1 <= NOT in1;
    out1 <= internal_signal1 AND in2;
End behavior;
```



VHDL Essentials

Process

- ❑ **Processes** contain the functional description of an architecture

```
out1 <= internal_signal1 AND in2; -- a simple process;
```

- ❑ A process can also be described by more than a line

```
process (A,B) --(A,B) is the sensitivity list of this process
Begin
    if (A > B) then
        Output <= A;
    else
        Output <= B;
    end if;
end process;
```

- ❑ During simulation, a process will be evaluated only when a change occurs in at least a signal of the **sensitivity list**. This shall include asynchronous signals (e.g. asynchronous reset) plus the process clock.
- ❑ Sensitivity list is only used for simulation. In synthesized circuits processes are constantly and concurrently executed.



VHDL Essentials

Process

- When an architecture is defined by several processes, these will infer circuits that will run concurrently. The order of the processes is not relevant

```
-- Ex1. Processes 1 and 2 run in parallel
```

```
C = B + 2; -- process 1
```

```
A = D + E; -- process 2
```


```
-- Ex2. This code cannot be synthesized
```

```
A = B + 2; -- process 1
```

```
A = C + 3; -- process 3
```

- In Ex2, while in C language this results $A = C + 3$, in VHDL this code cannot be synthesized because signal A is assigned two different values: $B+2$ and $C+3$
 
```
>> Error: Multiple sources for the same signal
```






VHDL Essentials

Synchronous Process

- ❑ Process output get updated just on the rising (falling) clock edge:
 - ❑ Thus, a memory element (biestable) is inferred at the output.
 - ❑ Process may have “if without else” statements → the biestable will remember the last value
 - ❑ Sensitivity list will include just async signals. Usually just reset and clk.
 
```
process(reset, clk)
begin
    if (reset = '1') then
        dout <= (others=>'0');
    elsif (clk'event and clk='1') then
        if (input_vld = '1') then
            dout <= din1 and din2;
        end if;
    end if;
end process;
```







VHDL Essentials

Sync vs Async Process
 
```
process(a, b)
begin
    if (a > b) then
        dout <= a;
    else
        dout <= b;
    end if;
end process;
```


 
```
process(clk)
begin
    if (clk'event and clk='1') then
        if (a > b) then
            dout <= a;
        else
            dout <= b;
        end if;
    end if;
end process;
```






VHDL Essentials

Decision and loop statements

❑ If - then - elsif - else

```
If (selection = '1') then  
    output <= A OR B;  
else  
    output <= A AND B;  
end if;
```

❑ Both OR and AND operators are inferred

 

```
if (condition1 = '1') then  
    C <= 0;  
elsif (condition2 = '1') then  
    C <= A;  
else  
    C <= B;  
end if;
```



VHDL Essentials

Decision and loop statements

- ❑ **Case** is useful for branching, where is more convenient than if/else

```
case option is
  when "00" =>
    out <= a;
  when "01"
    out <= b;
  when others -- all remainder cases: "10" and "11"
    out <= '0';
End case;
```

- ❑ Remember to add always `when others` to complete the definition of the case statement
- ❑ Although there is a **for** loop statement in VHDL, its function is quite different from the usual 'for' loops of C-like programming languages. Its use in VHDL is limited and out of the scope of this subject.



VHDL Essentials

Summary example

```
-- Bit multiplexer 2to1
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;      -- library (for logic operation)


ENTITY mux2to1 IS                  -- entity circuit declaration
    PORT (in_a:    IN  std_logic;  -- ports
          in_b:    IN  std_logic;
          sel:     IN  std_logic;
          output:  OUT std_logic);
END mux2to1;

ARCHITECTURE Behavioral OF mux2to1 IS --architecture declaration
BEGIN
    PROCESS (in_a, in_b, sel)      -- sensitivity list (async signals)
    BEGIN
        IF (sel='1') THEN
            output<=in_a;
        ELSE
            output<=in_b;
        END IF;
    END PROCESS;                  -- end of process
END Behavioral;                   -- end of behavioral architecture
```



VHDL Essentials

Hierarchical design: behavioral

 

```
entity foo_behab is
  Port ( clk : in  STD_LOGIC;
        reset : in  STD_LOGIC;
        a : in  STD_LOGIC_VECTOR (7 downto 0);
        b : in  STD_LOGIC_VECTOR (7 downto 0);
        dout : out STD_LOGIC);
end foo_behab;
```

```
architecture Behavioral of foo_behab is
  signal aux_signal: std_logic_vector (7 downto 0);
begin
```

```
  process (reset, clk)
  begin
    if (reset='1') then
      aux_signal <= (others=>'0');
    elsif (clk'event and clk='1') then
      if (a>b) then
        aux_signal <= a and b;
      else
        aux_signal <= a or b;
      end if;
    end if;
  end process;
```


```
  process (reset, clk)
  begin
    if (reset='1') then
      dout <= '0';
    elsif (clk'event and clk='1') then
      dout <= aux_signal(7) xor aux_signal(6)
        xor aux_signal(5) xor aux_signal(4)
        xor aux_signal(3) xor aux_signal(2)
        xor aux_signal(1) xor aux_signal(0);
    end if;
  end process;
```

```
end Behavioral;
```



VHDL Essentials

Hierarchical design: behavioral

 

```
entity foo_behab is
  Port ( clk : in  STD_LOGIC;
        reset : in  STD_LOGIC;
        a : in  STD_LOGIC_VECTOR (7 downto 0);
        b : in  STD_LOGIC_VECTOR (7 downto 0);
        dout : out STD_LOGIC);
end foo_behab;
```

```
architecture Behavioral of foo_behab is
  signal aux_signal: std_logic_vector (7 downto 0);
begin
```

```
  process (reset, clk)
  begin
    if (reset='1') then
      aux_signal <= (others=>'0');
    elsif (clk'event and clk='1') then
      if (a>b) then
        aux_signal <= a and b;
      else
        aux_signal <= a or b;
      end if;
    end if;
  end process;
```


```
  process (reset, clk)
  begin
    if (reset='1') then
      dout <= '0';
    elsif (clk'event and clk='1') then
      dout <= aux_signal(7) xor aux_signal(6)
        xor aux_signal(5) xor aux_signal(4)
        xor aux_signal(3) xor aux_signal(2)
        xor aux_signal(1) xor aux_signal(0);
    end if;
  end process;
```

```
end Behavioral;
```



VHDL Essentials

Hierarchical design: behavioral

 

```
entity foo_behab is
  Port ( clk : in  STD_LOGIC;
        reset : in  STD_LOGIC;
        a : in  STD_LOGIC_VECTOR (7 downto 0);
        b : in  STD_LOGIC_VECTOR (7 downto 0);
        dout : out STD_LOGIC);
end foo_behab;
```

```
architecture Behavioral of foo_behab is
  signal aux_signal: std_logic_vector (7 downto 0);
begin
```

```
  process (reset, clk)
  begin
    if (reset='1') then
      aux_signal <= (others=>'0');
    elsif (clk'event and clk='1') then
      if (a>b) then
        aux_signal <= a and b;
      else
        aux_signal <= a or b;
      end if;
    end if;
  end process;
```


```
  process (reset, clk)
  begin
    if (reset='1') then
      dout <= '0';
    elsif (clk'event and clk='1') then
      dout <= aux_signal(7) xor aux_signal(6)
        xor aux_signal(5) xor aux_signal(4)
        xor aux_signal(3) xor aux_signal(2)
        xor aux_signal(1) xor aux_signal(0);
    end if;
  end process;
```

```
end Behavioral;
```



VHDL Essentials

Hierarchical design: structural (i)

 

```
entity foo_hw1 is
  Port ( clk : in  STD_LOGIC;
        reset : in  STD_LOGIC;
        a : in  STD_LOGIC_VECTOR (7 downto 0);
        b : in  STD_LOGIC_VECTOR (7 downto 0);
        dout : out  STD_LOGIC_VECTOR (7 downto 0));
end foo_hw1;
```

```
architecture Behavioral of foo_hw1 is
```

```
begin
```

```
  process(reset, clk)
```

```
  begin
```

```
    if (reset='1') then
```

```
      dout <= (others=>'0');
```

```
    elsif (clk'event and clk='1') then
```

```
      if (a>b) then
```

```
        dout <= a and b;
```

```
      else
```

```
        dout <= a or b;
```

```
      end if;
```

```
    end if;
```


```
  end process;
```

```
end Behavioral;
```



VHDL Essentials

Hierarchical design: structural (ii)

 

```
entity foo_hw2 is
  Port (clk : in  STD_LOGIC;
        reset : in  STD_LOGIC;
        a : in  STD_LOGIC_VECTOR (7 downto 0);
        dout : out  STD_LOGIC);
end foo_hw2;

architecture Behavioral of foo_hw2 is
begin


  process (reset, clk)
  begin
    if (reset='1') then
      dout <= '0';
    elsif (clk'event and clk='1') then
      dout <= a(7) xor a(6) xor a(5) xor a(4)
              xor a(3) xor a(2) xor a(1) xor a(0);
    end if;
  end process;

end Behavioral;
```



VHDL Essentials

Hierarchical design: structural (iii)

 

```
entity foo_behab is
  Port ( clk : in  STD_LOGIC;
        reset : in  STD_LOGIC;
        a : in  STD_LOGIC_VECTOR (7 downto 0);
        b : in  STD_LOGIC_VECTOR (7 downto 0);
        dout : out  STD_LOGIC);
end foo_behab;
```

architecture Behavioral of foo_struct is

```
component foo_hw1 is
  Port ( clk : in  STD_LOGIC;
        reset : in  STD_LOGIC;
        a : in  STD_LOGIC_VECTOR (7 downto 0);
        b : in  STD_LOGIC_VECTOR (7 downto 0);
        dout : out  STD_LOGIC_VECTOR (7 downto 0));
end component;
```

```
component foo_hw2 is
  Port ( clk : in  STD_LOGIC;
        reset : in  STD_LOGIC;
        a : in  STD_LOGIC_VECTOR (7 downto 0);
        dout : out  STD_LOGIC);
end component;
```

```
signal aux_signal: std_logic_vector (7 downto 0);
```

begin

```
comp1: foo_hw1 port map(
  clk => clk,
  reset => reset,
  a => a,
  b => b,
  dout => aux_signal);
```


```
comp2: foo_hw2 port map(
  clk => clk,
  reset => reset,
  a => aux_signal,
  dout => dout);
```

end Behavioral;



VHDL Essentials

Hierarchical design: mixed style

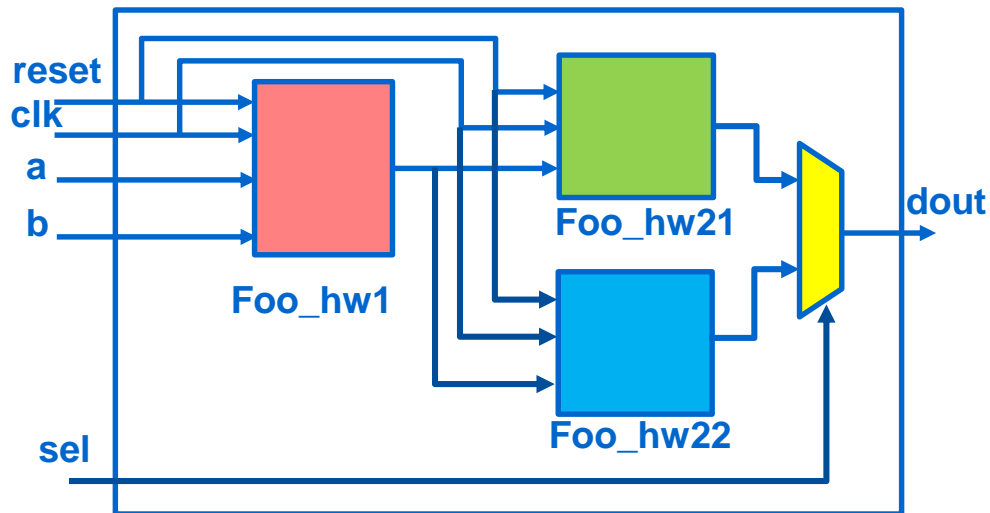

```
entity foo_behab is
  Port ( clk : in  STD_LOGIC;
        reset : in  STD_LOGIC;
        a : in  STD_LOGIC_VECTOR (7 downto 0);
        b : in  STD_LOGIC_VECTOR (7 downto 0);
        sel : in  STD_LOGIC;
        dout : out  STD_LOGIC);
end foo_behab;
```

```
architecture Behavioral of foo_struct is
  ...
```

```
begin
```

```
comp1: foo_hw1 port map(clk => clk,
                        reset => reset,
                        a => a,
                        b => b,
                        dout => aux_signal);
```

```
comp2: foo_hw2 port map(clk => clk,
                        reset => reset,
                        a => aux_signal,
                        dout => aux1);
```

```
comp3: foo_hw2 port map(clk => clk,
                        reset => reset,
                        a => aux_signal,
                        dout => aux2);
```

```
process (aux1, aux2)
begin
  if (sel='1') then
    dout <= aux2;
  else
    dout <= aux1;
  end if;
end process;
```

```
end Behavioral;
```