



# RTL Digital Systems with VHDL



# RTL Digital Systems with VHDL

---

## Index

- ❑ Abstraction levels in microprocessor-based digital systems
- ❑ Introduction to RTL digital systems
  - ❑ Combinational Systems. Examples and VHDL description
  - ❑ Sequential Systems. Examples and VHDL description




# RTL Digital Systems with VHDL

## Abstraction levels

Microprocessor-based systems can be described at different abstraction levels. Most commonly:

### System level

Controller, sensor, actuator...

 




# RTL Digital Systems with VHDL

## Abstraction levels

Microprocessor-based systems can be described at different abstraction levels. Most commonly:

System level      Chip Level

Processor, main memory, cache...

 



# RTL Digital Systems with VHDL

## Abstraction levels


Microprocessor-based systems can be described at different abstraction levels. Most commonly:

System level

Chip Level

Register Transfer Level (RTL)

Register, decoder, multiplexer...

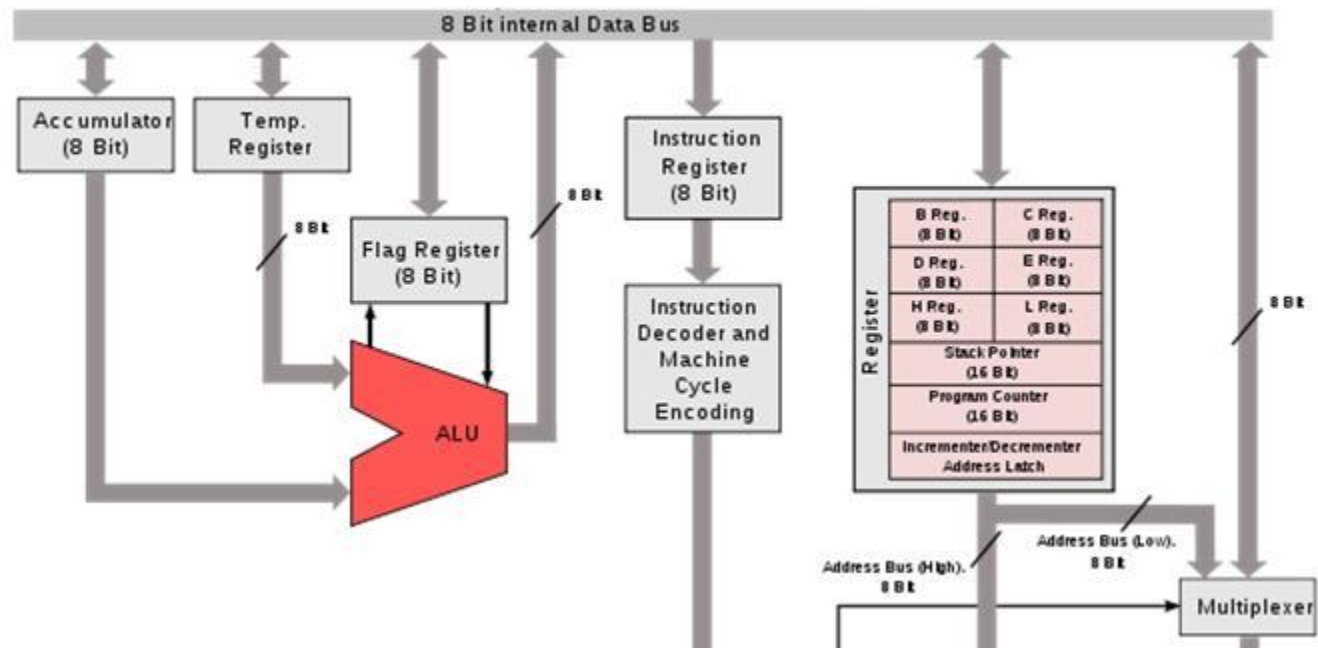



# RTL Digital Systems with VHDL

## Introduction to RTL digital systems

- ❑ We will focus on the synthesis of RTL digital systems with VHDL
- ❑ It is important to understand and to be capable of designing RTL circuits because they are essential in a large number of basic functions of a microprocessor-based hardware architecture
- ❑ RTL systems can be classified into the same categories as digital logic systems
  - ❑ Combinational systems. Output is a function of only present inputs
  - ❑ Sequential systems. Output is a function of present and past inputs.  
Sequential systems have memory and therefore possible states



# RTL Digital Systems with VHDL

## Combinational Systems

- ❑ Output is a function of only present inputs
- ❑ Output signals change as inputs change, only taking into consideration the delay due to the propagation through the logic gates and wires
- ❑ Most common combinational RTL digital systems
  - ❑ Multiplexer
  - ❑ Encoder
  - ❑ Decoder
  - ❑ Comparator
  - ❑ Tri-state buffer
  - ❑ ALU (Arithmetic Logic Unit)



# RTL Digital Systems with VHDL


## Multiplexer I: 2 inputs

### ❑ Function

$$\text{output} = (\text{sel} \text{ AND } \text{in\_a}) \text{ OR } (\overline{\text{sel}} \text{ AND } \text{in\_b})$$

### ❑ Utility: data-path circuit that allows signal selection

### ❑ Example of VHDL code

 

```
--Multiplexer of 2 binary inputs
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

--entity circuit declaration
ENTITY mux2to1 IS
    PORT (in_a:    IN    std_logic;
          in_b:    IN    std_logic;
          sel:     IN    std_logic;
          output:  OUT   std_logic);
END mux2to1;
```

```
ARCHITECTURE Behavioral OF mux2to1 IS
BEGIN
    PROCESS (in_a, in_b, sel)
    BEGIN
        IF (sel='1') THEN
            output<=in_a;
        ELSE
            output<=in_b;
        END IF;
    END PROCESS;
END Behavioral;
```





# RTL Digital Systems with VHDL

## Multiplexer II: More than 2 inputs

```
--Multiplexer of 3 binary inputs
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
--entity circuit declaration
ENTITY mux3to1 IS
    PORT (in_A:    IN  std_logic;
          in_B:    IN  std_logic;
          in_C:    IN  std_logic;
          SEL:     IN  std_logic_vector(1 downto 0);
          output:  OUT std_logic);
END mux3to1;


ARCHITECTURE Behavioral OF mux3to1 IS
BEGIN
    PROCESS (in_A, in_B, in_C, SEL)
    BEGIN
        CASE SEL IS
            WHEN "00"    => output <= in_A;
            WHEN "01"    => output <= in_B;
            WHEN others => output <= in_C;
        END CASE;
    END PROCESS;
END Behavioral;
```



# RTL Digital Systems with VHDL
 
## Encoder

- Utility: to encode information (to reduce the number of bits)
- Example of VHDL code



```
-- 8 to 3 encoder
LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;

ENTITY enc_8_3 IS
    PORT ( A: IN std_logic_vector(7 DOWNTO 0);
          Y: OUT std_logic_vector(2 DOWNTO 0);
          invalid: OUT std_logic);
END enc_8_3;

ARCHITECTURE Behavioral OF enc_8_3 IS

BEGIN
```


```
PROCESS (A)
BEGIN
    invalid <= '0';
    CASE A IS
        WHEN "00000001" => Y <= "000";
        WHEN "00000010" => Y <= "001";
        WHEN "00000100" => Y <= "010";
        WHEN "00001000" => Y <= "011";
        WHEN "00010000" => Y <= "100";
        WHEN "00100000" => Y <= "101";
        WHEN "01000000" => Y <= "110";
        WHEN "10000000" => Y <= "111";
        WHEN others      =>
            Y <= "000";
            invalid <= '1';
    END CASE;
END PROCESS;
END Behavioral;
```



# RTL Digital Systems with VHDL
 
## Decoder

- Utility: to decode information  
Example. To enable the proper device from the (codified) Address Bus
- Example of VHDL code



```
-- 3 to 8 decoder
LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;

ENTITY dec_3_8 IS
    PORT ( A: IN std_logic_vector(2 DOWNTO 0);
          Y: OUT std_logic_vector(7 DOWNTO 0));
END dec_3_8;

ARCHITECTURE Behavioral OF dec_3_8 IS
BEGIN
```

```
PROCESS (A)
BEGIN
    CASE A IS
        WHEN "000" => Y <= "00000001";
        WHEN "001" => Y <= "00000010";
        WHEN "010" => Y <= "00000100";
        WHEN "011" => Y <= "00001000";
        WHEN "100" => Y <= "00010000";
        WHEN "101" => Y <= "00100000";
        WHEN "110" => Y <= "01000000";
        WHEN others=> Y <= "10000000";
    END CASE;
END PROCESS;


END Behavioral;
```



# RTL Digital Systems with VHDL
 
## Comparator

- Utility: to compare multiple values
- Example of VHDL code



```
-- 2 words comparator
LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;

ENTITY comparator IS
    PORT ( A: IN std_logic_vector(7 DOWNTO 0);
          B: IN std_logic_vector(7 DOWNTO 0);
          enable: IN std_logic;
          AlessB: OUT std_logic;
          AequalB: OUT std_logic;
          AgreaterB: OUT std_logic);
END comparator ;

ARCHITECTURE Behavioral OF comparator IS
BEGIN
```


```
PROCESS(A, B, enable)
BEGIN
    IF (enable = '0') THEN
        AlessB<='0'; AequalB<= '0'; AgreaterB <= '0';
    ELSE
        IF ( A < B ) THEN --A less than B
            AlessB <= '1';
        ELSE
            AlessB <= '0';
        END IF;
        IF ( A > B ) THEN --A greater than B
            AgreaterB <= '1';
        ELSE
            AgreaterB <= '0';
        END IF;
        IF ( A = B ) THEN --A equals B
            AequalB <= '1';
        ELSE
            AequalB <= '0';
        END IF;
    END IF;
END PROCESS;
END Behavioral;
```



# RTL Digital Systems with VHDL
 
## Tri-state buffer

- Utility: to connect and disconnect signals. Example. When several signals must access a common line, to prevent short-circuits
- Example of VHDL code



```
-- tri-state binary buffer
LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;

ENTITY tristate IS
  PORT(enable: IN std_logic;
        A: IN  std_logic_vector(7 DOWNTO 0);
        Y: OUT std_logic_vector(7 DOWNTO 0));
END tristate;
```

```
ARCHITECTURE Behavioral OF tristate
IS
BEGIN
  PROCESS (A,enable)

  BEGIN
    IF (enable='1') THEN
      Y <= A;
    ELSE
      Y <= (others=>'Z');
    END IF;

  END PROCESS;
END Behavioral;
```




# RTL Digital Systems with VHDL

## ALU (Arithmetic Logic Unit)

- Utility: to perform arithmetic and logic operations
- Example of VHDL code

```
-- ALU (AND, OR, +, -)
LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;
USE IEEE.NUMERIC_STD.ALL;
ENTITY ALU IS
    PORT ( A: IN std_logic_vector(7 DOWNTO 0);
          B: IN std_logic_vector(7 DOWNTO 0);
          code_op: IN std_logic_vector(1 DOWNTO 0);
          result: OUT std_logic_vector(7 DOWNTO 0));
END ALU;

ARCHITECTURE Behavioral OF ALU IS
BEGIN
    PROCESS(A, B, code_op)
    BEGIN
        CASE code_op IS
            -- logic operations
            WHEN "00" => result <= A AND B;
            WHEN "01" => result <= A OR B;
            -- arithmetic operations
            WHEN "10" => result <= std_logic_vector(signed(A) + signed(B));
            WHEN others => result <= std_logic_vector(signed(A) - signed(B));
        END CASE;
    END PROCESS;
END Behavioral;
```

 



## Sequential Systems

Output is a function of present and past inputs.

- ❑ Sequential systems have memory and therefore possible states
- ❑ Sequential systems are mostly ruled by the clock signal
- ❑ Signals can be
  - ❑ Synchronous or clock-dependent
  - ❑ Asynchronous or clock-independent (typically only the asynchronous reset)

Most common RTL sequential digital systems


- ❑ D flip-flop
- ❑ Data registers
- ❑ Shift registers
- ❑ Counters



# RTL Digital Systems with VHDL
 
## D flip-flop

- ❑ Utility: to store a bit
- ❑ Flip-flops have two possible states:  
0 or 1
- ❑ Example of VHDL code



```
-- D-type flip-flop with asynchronous
-- reset, enable and synchronous reset
LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;
```

```
ENTITY Dff IS
    PORT ( clk:      IN  std_logic;
          a_reset: IN  std_logic;
          enable:  IN  std_logic;
          s_reset: IN  std_logic;
          din:     IN  std_logic;
          dout:    OUT std_logic);
END Dff;
```

```
ARCHITECTURE Behavioral OF Dff IS
BEGIN
```

```
PROCESS (a_reset, clk)
BEGIN
    IF (a_reset='1') THEN
        dout <= '0';
    ELSIF (clk'EVENT AND clk = '1') THEN
        IF (enable='1') THEN
            IF (s_reset='1') THEN
                dout <= '0';
            ELSE
                dout <= din;
            END IF;
        END IF;
    END IF;
END PROCESS;
END Behavioral;
```






# RTL Digital Systems with VHDL

## Data register

- Utility: to store a word
- VHDL code

 

```
-- 4-bits data register, parallel input/output,  
asynchronous reset, enable and synchronous reset
```

```
LIBRARY IEEE;
```

```
USE IEEE.STD_LOGIC_1164.ALL;
```

```
ENTITY dataregister IS
```

```
    PORT( clk      : IN  std_logic;  
          a_reset: IN  std_logic;  
          s_reset: IN  std_logic;  
          enable  : IN  std_logic;  
          din     : IN  std_logic_vector(3 DOWNTO 0);  
          dout    : OUT std_logic_vector(3 DOWNTO 0));
```

```
END dataregister;
```

```
ARCHITECTURE Behavioral OF dataregister IS  
BEGIN
```

```
    PROCESS (a_reset, clk)
```

```
    BEGIN
```

```
        IF (a_reset='1') THEN  
            dout <= (OTHERS=>'0');
```

```
        ELSIF (clk'EVENT AND clk='1') THEN
```

```
            IF (enable='1') THEN
```

```
                IF (s_reset='1') THEN  
                    dout <= (OTHERS=>'0');
```

```
                ELSE
```

```
                    dout <= din;
```

```
                END IF;
```

```
            END IF;
```

```
        END IF;
```

```
    END PROCESS;
```


```
END Behavioral;
```



# RTL Digital Systems with VHDL
 
## Shift register

- Utility: to store and shift a word
- VHDL code



```
-- 4-bits left shift data register, serial
-- input/output, parallel load, asynchronous reset
-- enable and synchronous reset
LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;
```

```
ENTITY shiftregister IS
    PORT( clk : IN std_logic;
          a_reset:IN std_logic;
          s_reset:IN std_logic;
          enable: IN std_logic;
          load : IN std_logic;
          data : IN std_logic_vector(3 DOWNTO 0);
          sin : IN std_logic;
          sout : OUT std_logic);
END shiftregister;
```

```
ARCHITECTURE Behavioral OF shiftregister IS
    SIGNAL reg: std_logic_vector(3 DOWNTO 0);

BEGIN
```

```
PROCESS (a_reset, clk)
BEGIN
    IF (a_reset='1') THEN
        reg <= (OTHERS=>'0');
    ELSIF (clk'EVENT AND clk='1') THEN
        IF (enable='1') THEN
            IF (s_reset='1') THEN
                reg <= (OTHERS=>'0');
            ELSIF (load='1') THEN
                reg <= data;
            ELSE
                -- left shift
                reg <= reg(2 DOWNTO 0) & sin;
            END IF;
        END IF;
    END IF;
END PROCESS;

sout <= reg(3); -- serial output


END Behavioral;
```



# RTL Digital Systems with VHDL
 
## Counter

- Utility: to count up and/or down  
Example: loops, iterated executions
- VHDL code



```
-- rising counter with asynchronous reset
LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;
USE IEEE.NUMERIC_STD.ALL;

ENTITY counter IS
    PORT (clk:      IN std_logic;
          load:     IN std_logic;
          a_reset:  IN std_logic;
          s_reset:  IN std_logic;
          enable:   IN std_logic;
          din:      IN std_logic_vector(2 downto 0);
          count:    OUT std_logic_vector(2 downto 0));
END counter;

ARCHITECTURE Behavioral OF counter IS
    SIGNAL count_aux: unsigned(2 downto 0);
BEGIN
```

```
PROCESS (clk, a_reset)
BEGIN
    IF (a_reset='1') THEN
        count_aux <= (OTHERS => '0');
    ELSIF (clk='1' AND clk'EVENT) THEN
        IF (enable='1') THEN
            IF (s_reset='1') THEN
                count_aux <= (OTHERS => '0');
            ELSIF (load='1') THEN
                count_aux <= unsigned(din);
            ELSE
                count_aux <= count_aux + 1;
            END IF;
        END IF;
    END IF;
END PROCESS;

count <= std_logic_vector(count_aux);
END Behavioral;
```